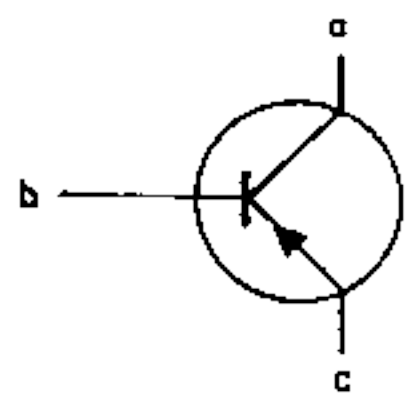


3.1.11.5

A que terminais correspondem as letras indicadas no seguinte transistor:



- A) a - emissor
b - base
c - colector }
- B) a - base
b - colector
c - emissor }
- C) a - colector
b - base
c - emissor }
- D) a - colector
b - emissor
c - base }